

# ENCM 467 Better "All The Equations (NA)"

## Tables

### Sign Conventions:

Parameter	NMOS	PMOS
Substrate	P-Type	N-Type
$\phi_f$	-	+
$Q_{Bo}, Q_B$	-	+
$V_{SB}$	+	-
$\gamma$	+	-
$V_{Th}$	+	-

## MOS Regions

### For nMOS, flip inequalities for pMOS

**Triode:**  $V_{ds} > 0$  &  $V_{gs} - V_{Th} > V_{ds}$

$$I_d = k'_n \frac{w}{L} [(V_{gs} - V_{Th})V_{ds} - \frac{V_{ds}^2}{2}]$$

**Saturation:**  $V_{ds} > 0$  and  $V_{ds} > V_{gs} - V_{Th}$


$$I_d = \frac{k'_n}{2} \frac{w}{L} (V_{gs} - V_{Th})^2$$

## MOS Capacitances

$$C_{sb} = C_j(L_s W + x_j W) + C_{jsw}(2L_s + W)$$

$(L_s W + x_j W)$  is the Kang textbooks area definition, Pg. 110

$$C_{jsw} = C_{jsw}' x_j$$

 

Pg. 112, Digital Integrated Circuits, Rabaey

### Junction Capacitances:

$$C_j = C_{j0} K_{eq}$$

$$K_{eq} = -\frac{\phi_o^m}{(V_2 - V_1)(1-m)} [(\phi_o - V_2)^{1-m} - (\phi_o - V_1)^{1-m}]$$

Find  $\phi_o$  in Diodes

### Sidewall Capacitance

$$C_{jsw}' = C_{j0sw} K_{eq}(sw)$$

$$C_{j0sw} = \sqrt{\frac{\epsilon_{si} q}{2} \frac{N_a(sw) N_d}{N_a(sw) + N_d} \frac{1}{\phi_{osw}}}$$

$$K_{eq}(sw) = -\frac{2\sqrt{\phi_{osw}}}{V_2 - V_1} (\sqrt{\phi_{osw} - V_2} - \sqrt{\phi_{osw} - V_1})$$

$$\phi_{osw} = \frac{kT}{q} \ln\left(\frac{N_a(sw) N_d}{n_i^2}\right)$$

$$V_{to(new)} = V_{to(n)} \pm \frac{q N_i}{C_{ox}}$$

NMOS: +Acceptors, -Donors

PMOS: +Donors, -Acceptors

## Constants

$$kT = 0.026eV$$

$$\frac{kT}{q} = \phi_T = V_T = 0.026V$$

$$k = 8.62 * 10^{-5} \frac{eV}{K} - \text{Boltzmann's Constant}$$

$$q = 1.602 * 10^{-19} C$$

$$n_i = 1.45 * 10^{10} cm^{-3} - \text{Intrinsic Conc. of Si at 300K}$$

$$\epsilon_o = 8.85 * 10^{-14} \frac{F}{cm}$$


$$\epsilon_{ox} = 3.9 * \epsilon_o \frac{F}{cm} - \text{Permittivity of SiO}_2$$

$$\epsilon_{si} = 11.8 * \epsilon_o \frac{F}{cm} - \text{Permittivity of Si}$$

$$\phi_f^{(gate)} = 0.55V$$

$$\int \frac{dx}{x(ax+b)} = \frac{1}{b} \ln\left(\frac{x}{ax+b}\right)$$

## MOSFETs

 

$$\phi_f = V_T \ln\left(\frac{n_i}{N_A}\right)$$

$$Q_B = \sqrt{2q N_A \epsilon_{si}} [-2\phi_f + V_{SB}]$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$V_{To} = \phi_{ms} - 2\phi_f - \frac{Q_{Bo}}{C_{ox}} - \frac{Q_{ox}}{C_{ox}}$$

$$V_{Th} = V_{To} + \gamma(\sqrt{|-2\phi_f + V_{SB}|} - \sqrt{|2\phi_f|})$$

$$\gamma = \frac{\sqrt{2q \epsilon_{si} N_A}}{C_{ox}}$$

$$Q_{ox} = q N_{ox}$$

$$k'_n = \mu_n C_{ox}$$

$$k_n = \frac{W}{L} k'_n$$

$$\lambda \text{ given: } I_{d,CLM} = I_d(1 + \lambda V_{ds})$$

$$g_m = g_{gs} = \frac{\partial I_d}{\partial V_{gs}} \big|_{V_{ds} \rightarrow \text{const}} = \frac{2I_d}{V_{gs} - V_{Th}}$$

$$g_{bs} = \frac{\partial I_d}{\partial V_{bs}} = g_{gs} \frac{\gamma}{2\sqrt{|-2\phi_f + V_{sb}|}} = \iota g_{gs}$$

$$g_{ds} = \lambda I_D \text{ (Saturation)}$$

$$I_D = g_{gs} V_{gs} + g_{bs} V_{bs} + \frac{V_{ds}}{r_{ds}}$$

### Unified Model:

$$I_d = \mu C_{ox} \frac{w}{L} [(V_{gs} - V_{Th}) V_{min} - \frac{V_{min}^2}{2}] (1 + \lambda V_{ds})$$

Where  $V_{min} = \min(V_{gs} - V_{th}, V_{ds}, V_{dsat})$

## Diodes

$$\phi_o = V_T \ln\left(\frac{N_a N_d}{n_i^2}\right)$$

$$I_d = I_s (e^{\frac{V_d}{n V_T}} - 1)$$

$$W_{dep} = \sqrt{\frac{2 \epsilon_{si} (\phi_o - V_d)}{q} \left(\frac{1}{N_d} + \frac{1}{N_a}\right)}$$

$$W_n = W_{dep} \frac{N_a}{N_d + N_a}$$

$$W_p = W_{dep} \frac{N_d}{N_d + N_a}$$

$$C_{jo} = \frac{\epsilon_{si} A}{W_{dep}}$$

$$C_j = C_{jo} \frac{1}{(1 - \frac{V_d}{\phi_o})^m}$$

$$C_d = \frac{(I_d + I_s) \tau_T}{V_T} \approx \frac{I_d \tau_T}{V_T}$$

$$C_d = C_{jo} \frac{1}{(1 - \frac{V_d}{\phi_o})^m} + \frac{\tau_T I_s}{V_T} e^{\frac{V_d}{n \phi_T}}$$

$$E_j = \sqrt{\frac{2q}{\epsilon_{si}} \frac{N_a N_d}{N_a + N_d} (\phi_o - V_d)}$$

$$Q_j = A_d \sqrt{2 \epsilon_{si} q \frac{N_a N_d}{N_a + N_d} (\phi_o - V_d)}$$

## Short Channel Effects

$L < 0.25 \mu m \rightarrow$  Short Channel

$$\mu_{n(eff)} = \frac{\mu_{no}}{1 + \Theta E_x} = \frac{\mu_{no}}{1 + \frac{\Theta \epsilon_{ox}}{t_{ox} \epsilon_{si}} (V_{gs} - V(x))}$$

$$m = \frac{3t_{ox}}{W} + 1$$

$$E_{sat} = \frac{2v_{sat}}{\mu}$$

$$v = \frac{\mu_{eff} E}{1 + E_{sat}}$$

$$I_d = \frac{I_{d(LongChannel)}}{1 + \frac{V_{ds}}{E_{sat} L}}$$

$$I_{dsat} = \frac{I_{dsat(LongChannel)}}{1 + \frac{(V_{gs} - V_{th})}{E_{sat} L}}$$

$$I_{dsat} = \frac{W v_{sat} C_{ox}}{m} (V_{gs} - V_{th}) \text{ Very Short Channel}$$

$$\frac{1}{V_{dsat}} = \frac{m}{V_{gs} - V_{th}} + \frac{1}{E_{sat} L}$$

## Short Channel Inverters

### CMOS:

$$G = -(g_{M1} + g_{M2})(R_{DS1} || R_{DS2})$$

$$g_m \approx k(V_{gs} - V_T)$$

$$R_{ds} \approx \frac{1}{\lambda I_d}$$

$$V_{th} = \frac{(V_{Tn} + \frac{V_{DSATn}}{2}) + r(V_{dd} - |V_{Tp}| + \frac{V_{DSATp}}{2})}{1+r}$$

$$\approx \frac{r V_{dd}}{1+r}$$

$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{E_{SATp} W_p}{E_{SATn} W_n}$$

$$\frac{k_p}{k_n} = \frac{V_{DSATn}(V_{th} - V_{Tn} - \frac{V_{DSATn}}{2})}{V_{DSATp}(V_{DD} - V_{Tn} - |V_{Tp}| + \frac{V_{DSATp}}{2})}$$

$$G \approx \frac{1+r}{(V_{th} - V_{Tn} - \frac{V_{DSATn}}{2})(\lambda_n - \lambda_p)}$$

$$NM_L = V_{th} - \frac{V_{dd} - V_{th}}{|G|}$$

$$NM_H = V_{dd} - V_{th}(1 + \frac{1}{|G|})$$

## Static Inverters

### General:

$$V_{IL} \text{ \& } V_{IH} @ \frac{dV_{out}}{dV_{in}} = -1$$

$$V_{OH} = V_{out}|_{V_{in}=V_{ss}}$$

$$V_{OL} = V_{out}|_{V_{in}=V_{dd}}$$

$$NM_L = |V_{IL} - V_{OL}|$$

$$NM_H = |V_{IH} - V_{OH}|$$

$$V_{ih} \rightarrow V_{out} = V_{in}$$

### Pseudo NMOS

$$k_r = k_n/k_p$$

$$V_{IL} = V_{TN} + \frac{V_{dd} - |V_{TP}|}{\sqrt{k_r^2 + k_r}}$$

$$V_{IH} = V_{TN} + \frac{2(V_{dd} - |V_{TP}|)}{\sqrt{3k_r}}$$

$$V_{OL} = \frac{V_{dd} - V_{TN}}{\sqrt{3k_r}}$$

$$V_{OH} = V_{dd} - (V_{dd} - |V_{tp}|)(1 - \sqrt{\frac{k_r}{k_r + 1}})$$

### Resistive Load NMOS Inverter:

$$V_{OH} = V_{dd}$$

$$V_{OL} = V_{dd} - V_{TN} + \frac{1}{k_n R_L} - \sqrt{(V_{dd} - V_{TN} + \frac{1}{k_n R_L})^2 - \frac{2V_{dd}}{k_n R_L}}$$

$$\approx \frac{V_{dd}}{1 + k_n R_L (V_{dd} - V_T)}$$

$$V_{IL} = V_{TN} + \frac{1}{k_n R_L}$$

$$V_{out}|_{V_{in}=V_{IL}} = V_{dd} - \frac{1}{2k_n R_L}$$

$$V_{IH} = V_{TN} + \sqrt{\frac{8V_{dd}}{3k_n R_L} - \frac{1}{k_n R_L}}$$

$$V_{out}|_{V_{in}=V_{IH}} = \sqrt{\frac{2V_{dd}}{3k_n R_L}}$$

$$V_{th} = V_{TN} - \frac{1}{k_n R_L} [1 - \sqrt{1 + 2k_n R_L (V_{dd} - V_{TN})}]$$

$$P_{DC(Avg)} = \frac{V_{dd}}{2} \frac{V_{dd} - V_{OL}}{R_L}$$

### CMOS Inverter:

$$V_{th} = \frac{V_{TN} + \sqrt{\frac{k_p}{k_n}} (V_{dd} - |V_{TP}|)}{(1 + \sqrt{\frac{k_p}{k_n}})}$$

$$\frac{k_p}{k_n} = \left( \frac{V_{th} - V_{TN}}{V_{dd} - V_{th} - |V_{TP}|} \right)^2$$

$$V_{IL} = \frac{2V_{out} - |V_{TP}| - V_{dd} + \frac{k_n}{k_p} V_{TN}}{(1 + \frac{k_n}{k_p})}$$

$$V_{IH} = \frac{V_{dd} - |V_{TP}| + \frac{k_n}{k_p} (2V_{out} + V_{TN})}{(1 + \frac{k_n}{k_p})}$$

Can approximate  $V_o = V_{dd}$ , or  $V_o = 0$  for the above or find exact by substituting back into the  $I_{d1} = I_{d2}$  equation.

Power in CMOS:

$$P_{dyn} = C_L V_{dd}^2 f_{0 \rightarrow 1}$$

$$P_{sc} = t_{sc} V_{dd} i_{peak} f$$

$$t_{sc} = \frac{V_{dd} - 2V_T}{V_{dd}} \left( \frac{t_r(f)}{0.8} \right)$$

$$P_{TOTAL} = P_{DYN} + P_{SC} + P_{STATIC}$$

## Transient MOS Inverters

$$R_n = \frac{1}{k_n (V_{dd} - V_{TN})} = \frac{V_{ds}}{I_{ds}}$$

$$R_p = \frac{1}{k_p (V_{dd} - |V_{TP}|)} = \frac{V_{sd}}{I_{sd}}$$

$$\tau \propto \frac{VC}{I} \propto RC$$

$$\tau_n = R_n C_L \text{ From ENEL 343}$$

$$\tau_p = R_p C_L$$

$$\tau_{PHL} = \ln(2) \tau_n = \frac{0.69 C_L}{k_n (V_{dd} - V_{tn})}$$

$$\tau_{PLH} = \ln(2) \tau_p = \frac{0.69 C_L}{k_p (V_{dd} - |V_{tp}|)}$$

$$t_p = \frac{1}{2} (\tau_{PHL} + \tau_{PLH})$$

$$t_r = 2.2 \tau_p = \frac{2.2 C_L}{k_p (V_{dd} - |V_{tp}|)} \quad 10\% \text{ to } 90\%$$

$$t_f = 2.2 \tau_n = \frac{2.2 C_L}{k_n (V_{dd} - V_{tn})} \quad 90\% \text{ to } 10\%$$

$$f_{max} = \frac{1}{t_r + t_f}$$

$$C_L = C_{gd,n} + C_{gd,p} + C_{db,n} + C_{db,p} + C_w + C_g$$

### Short Channel:

$$R_{n,p} = \frac{3V_{dd}}{4I_{DSAT}} (1 - \frac{7}{9} \lambda V_{dd})$$

$$I_{DSAT} = k V_{DSAT} (V_{dd} - V_t - \frac{V_{DSAT}}{2})$$

$$\tau_{PHL} = \frac{0.52 V_{dd} C_L}{I_{DSAT,n}}$$

$$\tau_{PLH} = \frac{0.52 V_{dd} C_L}{I_{DSAT,p}}$$

## Inverter Chain Sizing

$f \rightarrow$  Device Size Increase per Inverter

$$f = \sqrt[N]{\frac{C_L}{C_{g,1}}} = \sqrt[N]{F}$$

$$f_{opt} = 3.6$$

$$N_{opt} = \frac{\ln(C_{out}/C_{in})}{\ln(3.6)}$$

$$t_p = N t_{po} (1 + \frac{\sqrt[N]{F}}{\gamma})$$

## Gate Chain Sizing

$$g = \frac{C_{Gate}}{C_{Inverter}}$$

$$g_{NAND} = \frac{n+2}{3}$$

$$g_{NOR} = \frac{2n+1}{3}$$

$$g_{XOR2} = 4$$

$$g_{XOR3} = 12$$

$$g_{NOT} = 1$$

$$p = \frac{R_{gate} C_{d,gate}}{R_{inv} C_{d,inv}}$$

$$p_{Inverter} = 1$$

$$p_{NAND} = n$$

$$p_{NOR} = n$$

$$p_{XOR, XNOR} = n 2^{n-1}$$

$$t_p = t_{po} (\sum_{j=1}^N p_j + \frac{N \sqrt[N]{H}}{\gamma})$$

$$b_i = \frac{C_{path} + C_{offpath}}{C_{path}} \text{ How many gates the output feeds into.}$$

$$G = g_1 g_2 g_3 \dots g_n \text{ each } g_i \text{ is only the specific gate passed through.}$$

$$B = b_1 b_2 b_3 \dots b_n$$

$$H = GFB$$

$$h_{opt} = \sqrt[N]{H} \text{ N is how many rows of Gates.}$$

$$C_x = \frac{g_x C_{out} b_x}{h_{opt}}, \text{ This is the Sizing of each Gate, and } C_x \text{ for one gate is } C_{out} \text{ for the one prior.}$$

## Sequential Logic

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$

$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$

## CMOS Logic Gates

### N Input NOR:

$$V_{th} = \frac{V_{dd} - |V_{tp}| + N V_{tn} \sqrt{k_n/k_p}}{1 + N \sqrt{k_n/k_p}}$$

### N Input NAND:

$$V_{th} = \frac{V_{dd} - |V_{tp}| + \frac{1}{N} V_{tn} \sqrt{k_n/k_p}}{1 + \frac{1}{N} \sqrt{k_n/k_p}}$$

$$\text{Series MOS: } k_{n,p} = k_{n,p1} / k_{n,p2}$$

$$\text{Parallel MOS: } k_{n,p} = k_{n,p1} + k_{n,p2}$$

$$R_{eq} \propto \frac{1}{\frac{W}{L}}$$

$$R_{opt}(PUN) \propto \frac{L}{2W}$$

$$R_{opt}(PDN) \propto \frac{L}{W}$$

$$t_{elmore} = R_1 C_1 + (R_1 + R_2) C_2 \dots + (R_1 + R_2 + \dots + R_n) C_n$$